

SIMULATION AND IMPLEMENTATION OF SEQUENTIAL LOGIC CIRCUITS

AIM:

To simulate and synthesis SR, JK, T, D - FLIPFLOP, COUNTER DESIGN using Xilinx ISE.

APPARATUS REQUIRED:

Xilinx 14.7 Spartan6 FPGA

PROCEDURE:

STEP:1

Start the Xilinx navigator, Select and Name the New project.

STEP:2

Select the device family, device, package and speed.

STEP:3

Select new source in the New Project and select Verilog Module as the Source type.

STEP:4

Type the File Name and Click Next and then finish button. Type the code and save it.

STEP:5

Select the Behavioral Simulation in the Source Window and click the check syntax.

STEP:6

Click the simulation to simulate the program and give the inputs and verify the outputs as per the truth table.

STEP:7

Select the Implementation in the Sources Window and select the required file in the Processes Window.

STEP:8

Select Check Syntax from the Synthesize XST Process. Double Click in the FloorplanArea/IO/Logic-Post Synthesis process in the User Constraints process group. UCF(User constraint File) is obtained.

STEP:9

In the Design Object List Window, enter the pin location for each pin in the Loc column Select save from the File menu.

STEP:10

Double click on the Implement Design and double click on the Generate Programming File to create a bitstream of the design.(.v) file is converted into .bit file here.


STEP:11

On the board, by giving required input, the LEDs starts to glow light, indicating the output.

LOGIC DIAGRAM:

SR FLIPFLOP:

SR Flip Flop

 


Sno	S	R	Q	Q'	State
1	1	0	1	0	Q is set to 1
2	1	1	1	0	No change
3	0	1	0	1	Q' is set to 1
4	1	1	0	1	No change
5	0	0	1	1	Invalid

VERILOG CODE:

```
module srflipflop(clk,res,s,r,q);  
input clk,res,s,r;  
output reg q;  
always@(posedge clk)  
begin  
if(res)  
q<=1'b0;  
else begin  
case({s,r})  
2'b00:q<=q;  
2'b01:q<=1'b0;  
2'b10:q<=1'b1;  
2'b11:q<=1'bx;  
default:q<=1'bx;  
endcase  
end  
end  
endmodule
```

OUTPUT WAVEFORM :

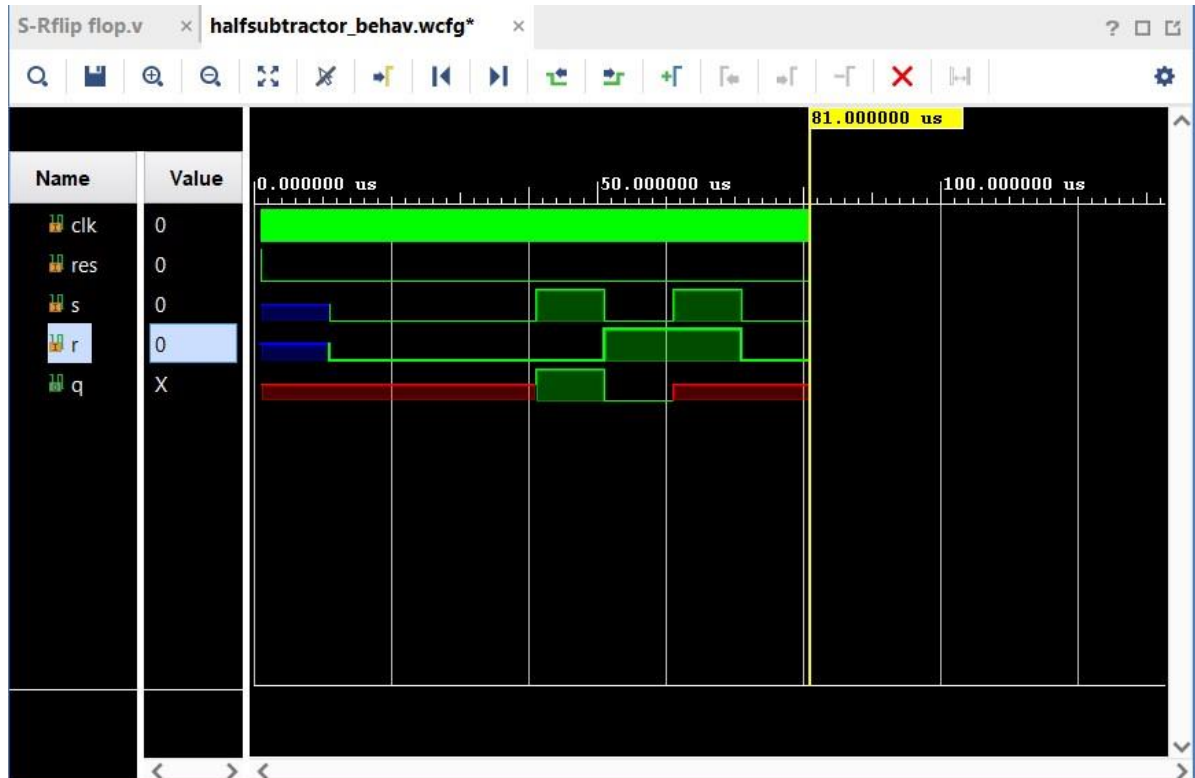

LOGIC DIAGRAM:

JK FLIPFLOP:


Truth Table

J	K	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	$\overline{Q_0}$ (toggles)

VERILOG CODE:

```
module jk(clk,res,j,k,q);  
input clk,res,j,k;  
output reg q;  
always@(posedge clk)  
begin  
if(res)  
q<=1'b0;  
else begin  
case({j,k})  
2'b00:q<=q;  
2'b01:q<=1'b0;  
2'b10:q<=1'b1;  
2'b11:q<=~q;  
default:q<=~q;  
endcase  
end  
end  
endmodule
```

OUTPUT WAVEFORM :

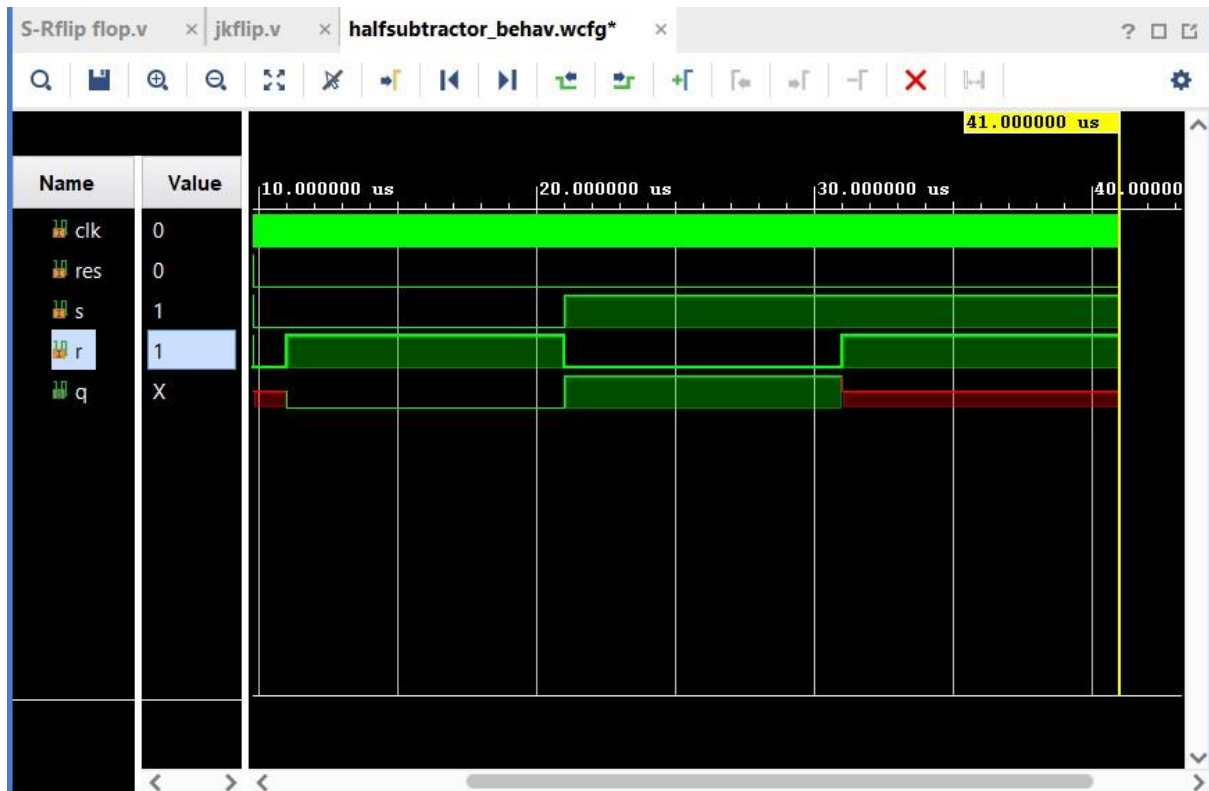

LOGIC DIAGRAM:

T FLIPFLOP:

Input	Outputs	
	Present State	Next State
T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

VERILOG CODE:


```
module tflipflop(clk,res,q,t);
input clk,res,t;
output reg q;
always@(posedge clk)
begin
if(res)
q<=1'b0;
else
begin
if(res)
q<=0;
else if(t)
q<=~q;
else
q<=q;
end
end
end
```

end

end

endmodule

OUTPUT WAVEFORM :

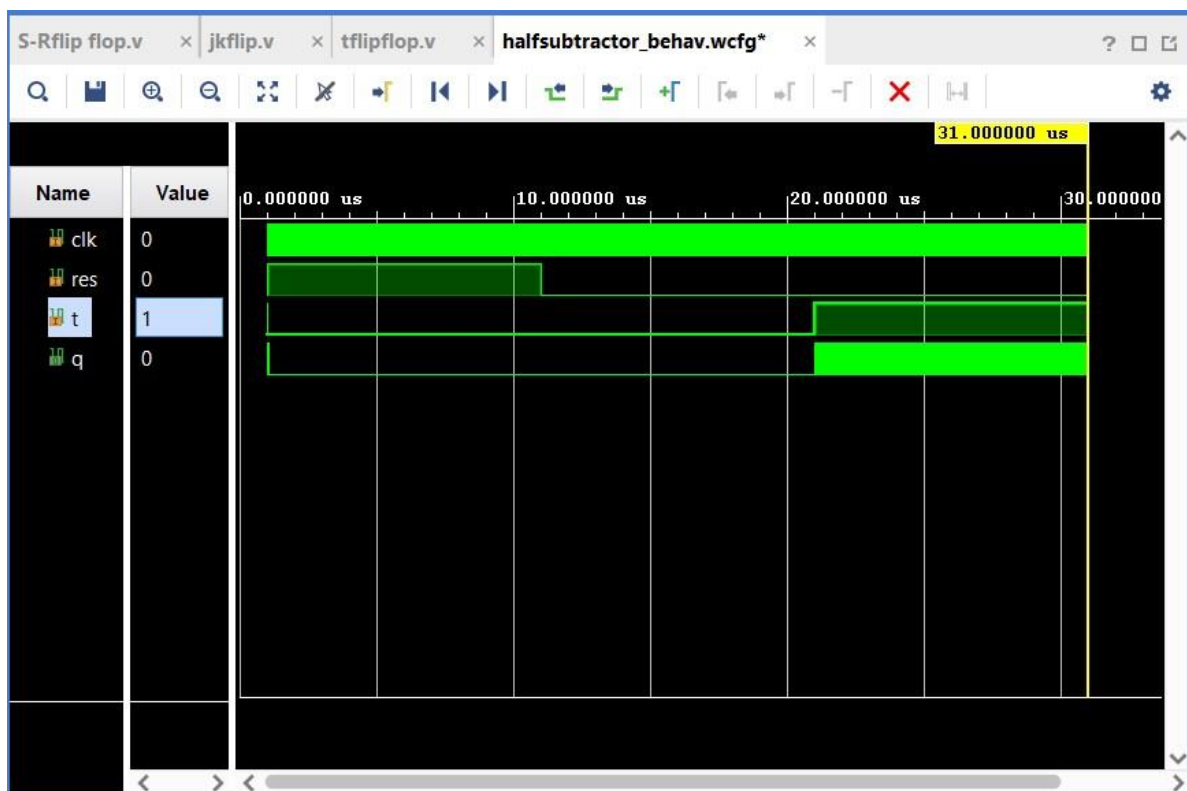

LOGIC DIAGRAM:

D FLIPFLOP:

D	Q(Current)	Q(n+1) (Next)
0	0	0
0	1	0
1	0	1
1	1	1

VERILOG CODE:

```
module dflipflop(c,r,d,q);
```

```
input c,r,d;
```

```
output reg q;
```

```
always @(posedge c)
```

```
begin
```

```
if(r)
```

```
q<= 1'b0 ;
```


```
else
```

```
q<=d;
```

```
end
```

```
endmodule
```

OUTPUT WAVEFORM :

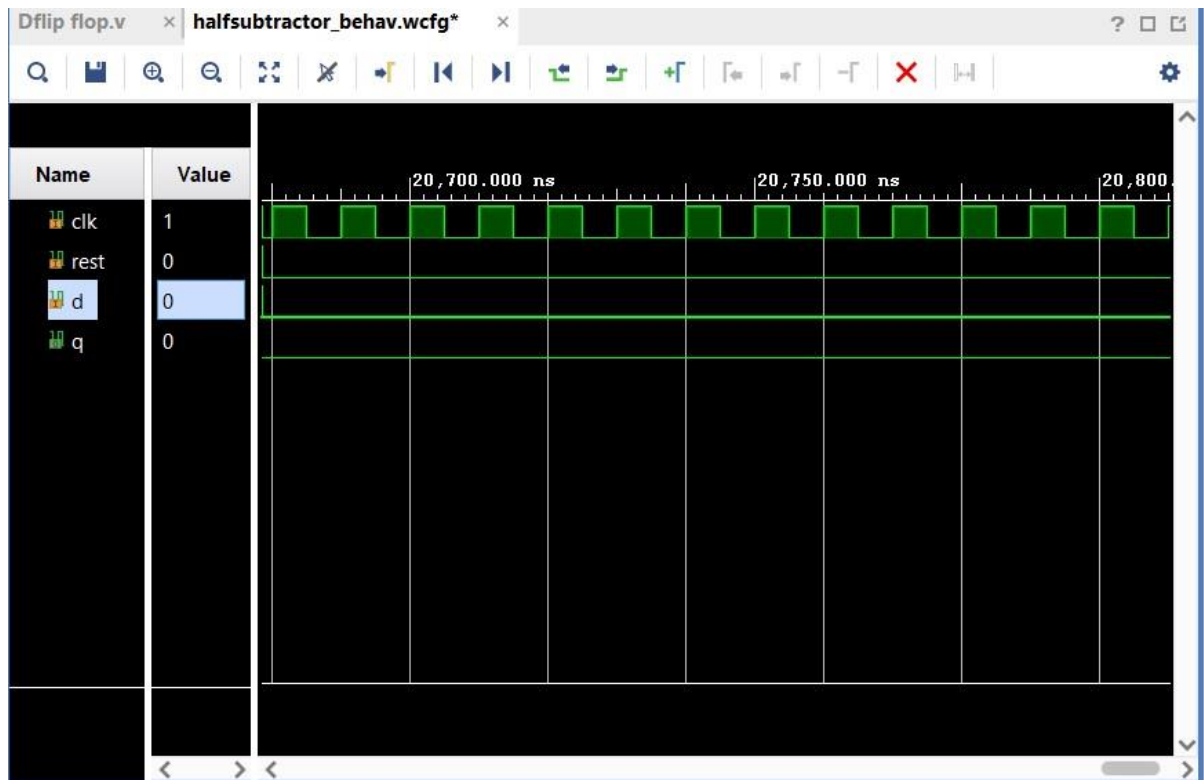

LOGIC DIAGRAM:

COUNTER:


Rst	CLK	O3	O2	O1	O0
1	↑	0	0	0	0
0	↑	0	0	0	1
0	↑	0	0	1	0
0	↑	0	0	1	1
0	↑	0	1	0	0
0	↑	0	1	0	1
0	↑	0	1	1	0
0	↑	0	1	1	1
0	↑	1	0	0	0
0	↑	1	0	0	1
0	↑	1	0	1	0
0	↑	1	0	1	1
0	↑	1	1	0	0
0	↑	1	1	0	1
0	↑	1	1	1	0
0	↑	1	1	1	1
0	↑	0	0	0	0

VERILOG CODE:

UP COUNTER:

```
module upcounter(clk,rest,count);  
input clk,rest;  
output [3:0]count;  
reg[3:0]count;  
always@(posedge clk)  
begin  
if(rest)  
count<=4'b0;  
else  
count<=count+1;  
end  
endmodule
```

OUTPUT WAVEFORM :

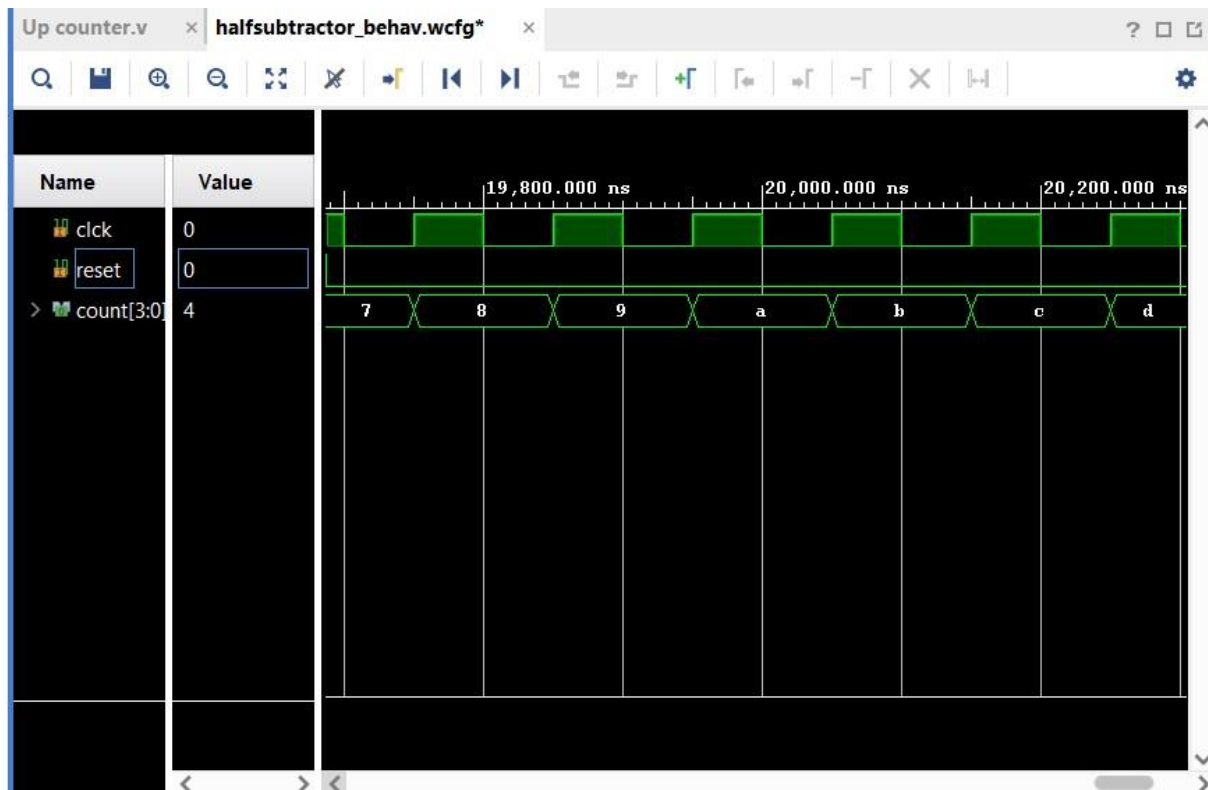

VERILOG CODE:

DOWN COUNTER:


```
module downcounter(clk,rest,count);  
input clk,rest;  
output [3:0]count;  
reg[3:0]count;  
always@(posedge clk)  
begin  
if(rest)  
count<=4'b0;  
else
```

```
count<=count-1;
```

```
end
```

```
endmodule
```

OUTPUT WAVEFORM :

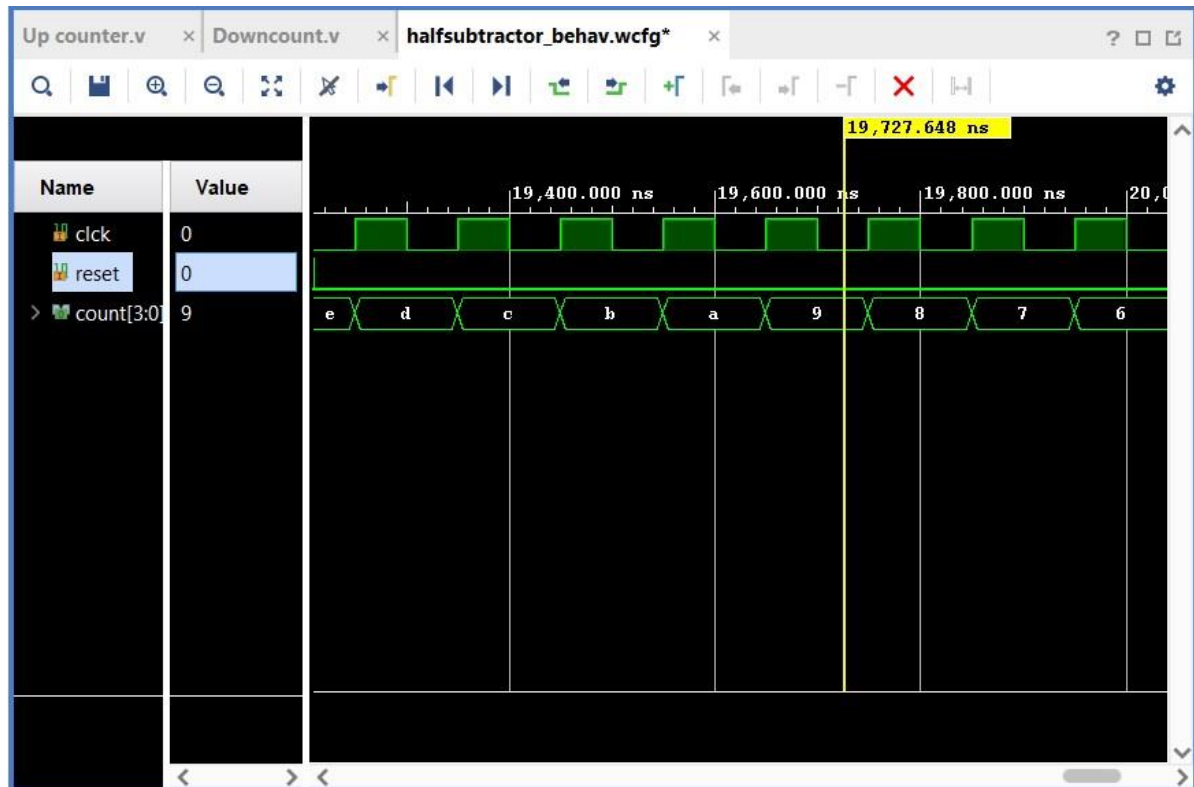

VERILOG CODE:

MOD 10:

```
module mod10(clk,res,count);
```

```
input clk,res;
```

```
output [3:0]count;
```

```
reg [3:0]count;
```

```
always@(posedge clk)
```


```
begin
```

```

if(res|count==4'd9)
count<=4'b0;
else
count<=count+1;
end
endmodule

```

OUTPUT WAVEFORM :

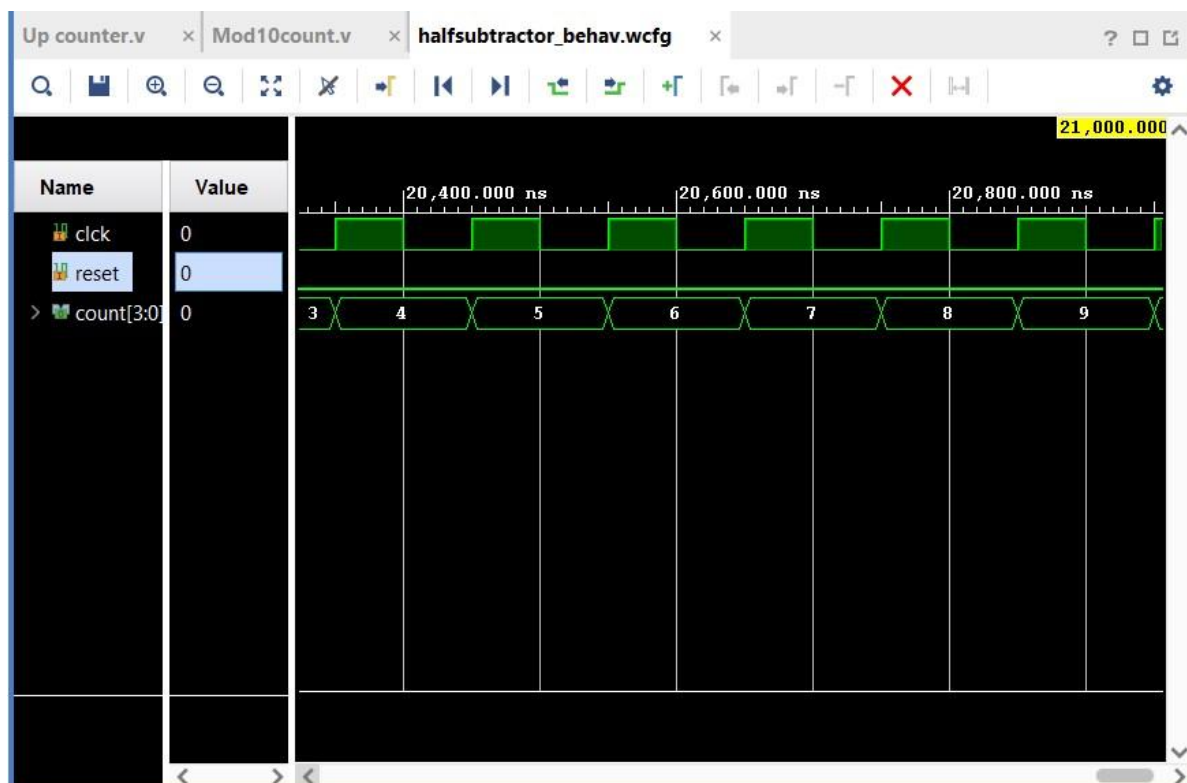

VERILOG CODE:

RIPPLE CARRY COUNTER:

Verilog Code for jkff: (Behavioural model)


```
module jkff(j,k,clock,reset,q,qb);  
input j,k,clock,reset;  
output reg q,qb;  
always@(negedge clock)  
begin  
case({reset,j,k})  
3'b100 :q=q;  
3'b101 :q=0;  
3'b110 :q=1;  
3'b111 :q=~q;  
default :q=0;  
endcase  
qb<=~q;  
end  
endmodule
```

Verilog Code for 4-bit Asynchronous up counter using JK-FF (Structural model):

```
module ripple_count(j,k,clock,reset,q,qb);  
input j,k,clock,reset;  
output wire [3:0]q,qb;  
  
jkff JK1(j,k,clock,reset,q[0],qb[0]);  
jkff JK2(j,k,q[0],reset,q[1],qb[1]);  
jkff JK3(j,k,q[1],reset,q[2],qb[2]);
```

```
jkff JK4(j,k,q[2],reset,q[3],qb[3]);  
endmodule
```

OUTPUT WAVEFORM :

 

RESULT:

The simulation and synthesis SR FLIPFLOP, JK FLIPFLOP, T FLIPFLOP, D FLIPFLOP, COUNTERS by running successfully using Xilinx ISE.